

Name: Kirsten Kajubi
Course: CIS 310
Assignment 3: 8 bit processor
Date: 04/20/2026

Github Repo Link: <https://github.com/KirstenKajubi/Assignment-3-8-bit-processor>

Design and Implementation of an 8-Bit Multicycle Processor

1. Introduction

In this project, I designed and implemented an 8-bit multicycle processor using Digital logic simulation. The goal was to build a functional CPU capable of executing simple arithmetic instructions while demonstrating proper coordination between datapath components and a control unit.

The processor follows a multicycle architecture, where each instruction is executed over four stages: fetch, decode, execute, and writeback. This design emphasizes the importance of timing, synchronization, and control signal generation in processor design.

2. Instruction Format

The processor uses an 8-bit instruction format divided into two fields:

- Upper 4 bits: Opcode
- Lower 4 bits: Immediate value

Example:

0x12 = 0001 0010

↑ ↑

opcode immediate

In this implementation, the opcode **0001** represents the ADD instruction.

3. Processor Architecture

The processor consists of the following components:

3.1 Program Counter (PC)

- Stores the address of the current instruction
- Increments only during the fetch stage
- Controlled using the signal **PC_inc**

3.2 Instruction Memory (ROM)

- Stores the program instructions
- Uses a 3-bit address space (8 instructions total)
- Outputs 8-bit instruction values

3.3 Instruction Register (IR)

- Stores the current instruction
- Loads only during the fetch stage (**IR_load**)
- Keeps the instruction stable throughout execution

3.4 Control Unit

- Implements a 4-stage multicycle control:
 - Fetch
 - Decode
 - Execute
 - Writeback
- Built using a one-hot state machine with flip-flops
- Uses a decoder to interpret opcode
- Generates control signals:
 - **IR_load**
 - **PC_inc**
 - **add_execute**
 - **add_writeback**

3.5 Arithmetic Logic Unit (ALU)

- Performs arithmetic operations (addition in this design)
- Inputs:
 - A: Current register value
 - B: Zero-extended immediate value
- Output:
 - Result sent to the register

3.6 Register

- Stores the result of computations
- Updates only during the writeback stage
- Controlled by:
 - `en` (enable signal from `add_writeback`)
 - `clk`

4. Datapath Overview

The datapath is structured as follows:

PC → ROM → IR → Control Unit

IR → ALU → Register → ALU (feedback loop)

Operation flow:

- The PC selects an instruction from ROM
- The instruction is loaded into the IR
- The control unit decodes the instruction
- The ALU performs computation
- The result is stored in the register and fed back for the next operation

5. Control Logic Design

The control unit operates using a one-hot state machine:

Cycle 1: `inst_fetch`

Cycle 2: `inst_decode`

Cycle 3: `inst_exec`

Cycle 4: `write_back`

Control signals are defined as:

- `IR_load` = `inst_fetch`
- `PC_inc` = `inst_fetch`
- `add_execute` = `inst_exec` AND (`opcode == ADD`)
- `add_writeback` = `write_back` AND (`opcode == ADD`)

This ensures proper sequencing and synchronization between control and datapath components.

6. Program Execution

The program loaded into ROM is:

ADD 2
ADD 3
ADD 1
ADD 4

Machine code representation:

0x12
0x13
0x11
0x14

7. Results

The register output (**RegQ**) was monitored during execution of the program.

The processor produced the following sequence:



$0 \rightarrow 2 \rightarrow 5 \rightarrow 6 \rightarrow 10$

This matches the expected results:

- $\text{ADD } 2 \rightarrow 0 + 2 = 2$
- $\text{ADD } 3 \rightarrow 2 + 3 = 5$
- $\text{ADD } 1 \rightarrow 5 + 1 = 6$
- $\text{ADD } 4 \rightarrow 6 + 4 = 10$

These results confirm that:

  - Instructions are fetched correctly
- The control unit properly sequences execution
- The ALU performs correct computations
- The register updates only during the writeback stage



8. Challenges and Debugging

Several challenges were encountered during development:

- Synchronizing the PC, IR, and control unit timing
- Preventing the PC from incrementing every clock cycle
- Ensuring instructions remained stable across multiple stages
- Correctly implementing writeback timing
- Debugging incorrect ALU and register connections

These issues were resolved by:

- Using ROM instead of RAM for stable instruction storage
- Introducing `PC_inc` to control when the PC increments
- Connecting `IR_load` to the fetch stage
- Carefully verifying signal timing and data flow

9. Conclusion

This project successfully demonstrates the design and implementation of an 8-bit multicycle processor. The processor correctly executes a sequence of instructions using a structured datapath and synchronized control unit.

The final implementation highlights key computer architecture concepts, including instruction execution timing, control signal generation, and datapath coordination.